

Lab 4: Keypad

ECE 3720



Preview


A keypad will be connected to the board and the output will be displayed as a binary on microcontroller output pins.

| Topic | Slide |
|-----------------|----------|
| Keypad Overview | <u>3</u> |
| Lab Goals | <u>5</u> |
| Key Mask | <u>6</u> |



Keypad Overview

- Each button on the keypad is a button just like the one used in Lab 2.
 - This necessitates the use of pulling resistors
- This shows one method of setting up a keypad
 - Each column is set as input and pulled up to digital high
 - Each row is set to digital low one at a time (the rest are set to high)
 - The inputs (columns) are scanned and if one reads low, that means the button corresponding to the row and column is pressed
- How could we change this?

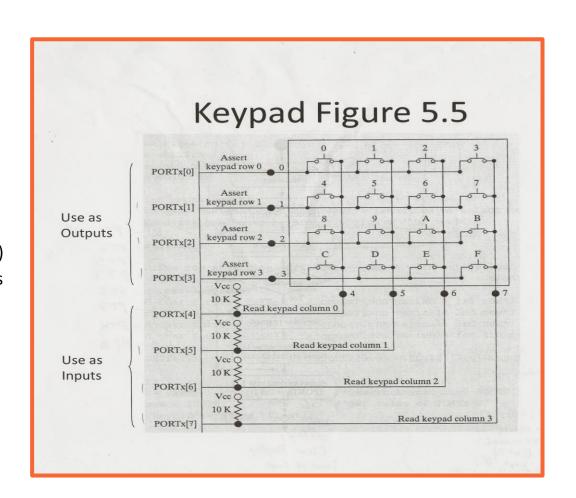



Keypad

- Datasheet available on Canvas and <u>here</u>
 - This will show you the pinouts for this specific keypad
 - See the *How it Works* section on page 2
- It is the user's responsibility to supply the necessary pulling resistors.






Lab Goals

- The keypad will be connected as shown to the right
 - You'll need to refer to the datasheet for the appropriate pins on the keypad
 - You will use internal pull-down resistors (taught in Lab 2) instead of pull-ups shown earlier
- 4 LEDs will be connected to separate outputs of the MC and indicate which key was pressed.
- When you push a key, the AD2 will display that key's value in binary via Static IO

Simple Diagram

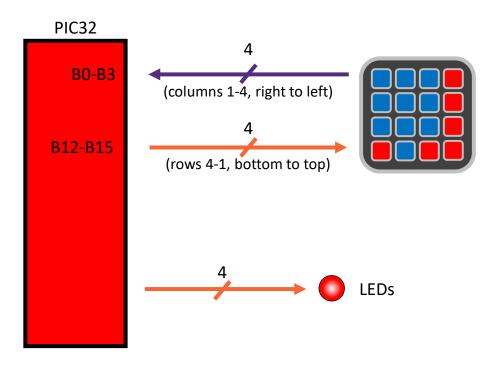





Key Mask

- The mask assumes you connect the wires EXACTLY as described on the previous slide
- The purpose of the mask is to simplify the setting of each column bit and scanning the rows
 - Each value corresponds to a specific row/column combo that will only be true when a button is pushed
 - Think (for) loops
 - You may need to use bit-masking when scanning the inputs (input&OxF)
- key_mask gives you the corresponding output for each key
 - Note that A-D, *, and # have been replaced with 10-15. We can't display letters and symbols on LEDs